 




Лингвистические средства проектирования


Лекция 4

Последовательные и параллельные операторы



Вывод данных и управление процессом моделирования (1)
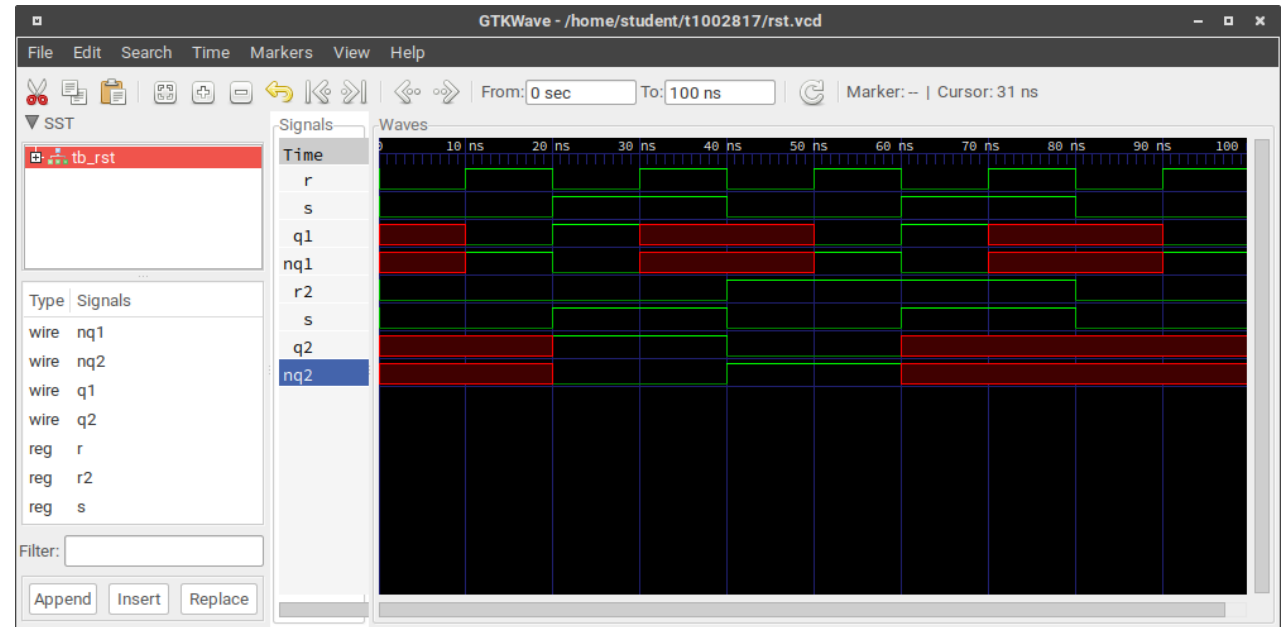
```
module rstrig(r, s, q, nq);  
  input r, s;  
  output reg q, nq;  
  
  always @(r, s) begin  
    case ({r, s})  
      1: {q, nq} <= 2;  
      2: {q, nq} <= 1;  
      3: begin  
          {q, nq} <= 2'bxx;  
          $display("Error [%m]! Illegal seq at %0t!", $realtime);  
        end  
    endcase  
  end  
endmodule
```



Вывод данных и управление процессом моделирования (2)

```
module rstrig(r, s, q, nq);  
  input r, s;  
  output reg q, nq;
```

```
  reg state = 0;
```

```
  always @(r, s) begin
```

```
    case ({r, s})
```

```
      0: if (state == 1)
```

```
        {q, nq} <= 2'bxx;
```

```
        1: {q, nq} <= 2;
```

```
        2: {q, nq} <= 1;
```

```
        3: begin
```

```
          $display("Error [%m]! Illegal seq at %0t!", $realtime);
```

```
          state <= 1;
```

```
          {q, nq} <= 0;
```

```
        end
```

```
      endcase
```

```
    end
```

```
  endmodule
```

```
1: {state, q, nq} <= 2;
```

```
2: {state, q, nq} <= 1;
```




```
1: {q, nq, state} <= 2 << 1;
```

```
2: {q, nq, state} <= 1 << 1;
```



Вывод данных и управление процессом моделирования (3)

```
module rstrig(r, s, q, nq);  
  input r, s;  
  output reg q, nq;  
  
  reg state = 0;  
  
  always @(r, s) begin  
    case ({r, s})  
      0: if (state == 1)  
          {q, nq} <= 2'bxx;  
      1: {q, nq} <= 2;  
      2: {q, nq} <= 1;  
      3: begin  
          $display("Error [%m]! Illegal seq at %0t!", $realtime);  
          state <= 1;  
          {q, nq} <= 0;  
          $finish;  
        end  
    end  
end
```

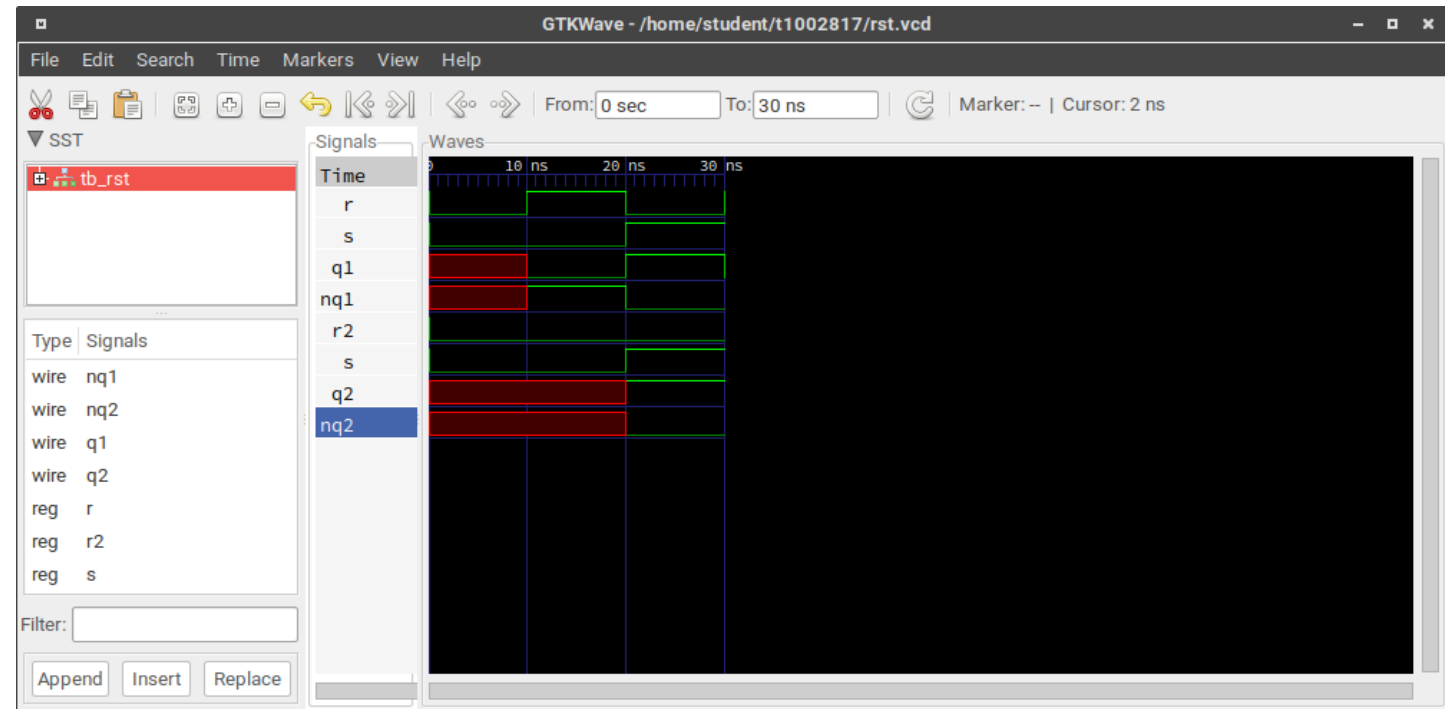

Особенности написания кода

```
`define STATUS_OK    0
`define STATUS_ERROR 1

module rstrig(r, s, q, nq);
  input r, s;
  output reg q, nq;

  reg state = `STATUS_OK;




  always @(r, s) begin
    case ({r, s})
      0: if (state == `STATUS_ERROR)
          {q, nq} <= 2'bxx;
      1: {state, q, nq} <= 2;
      2: {state, q, nq} <= 1;
      3: begin
          $display("Error [%m]! Illegal seq at %0t!", $realtime);
          state <= `STATUS_ERROR;
          {q, nq} <= 0;
        end
    end
  end
```

Последовательные операторы: циклы forever и repeat (1)

```
initial begin
  repeat (10)
    #5 C = ~C;
end
```

```
initial begin
  forever
    repeat (10)
      #5 C = ~C;
end
```

 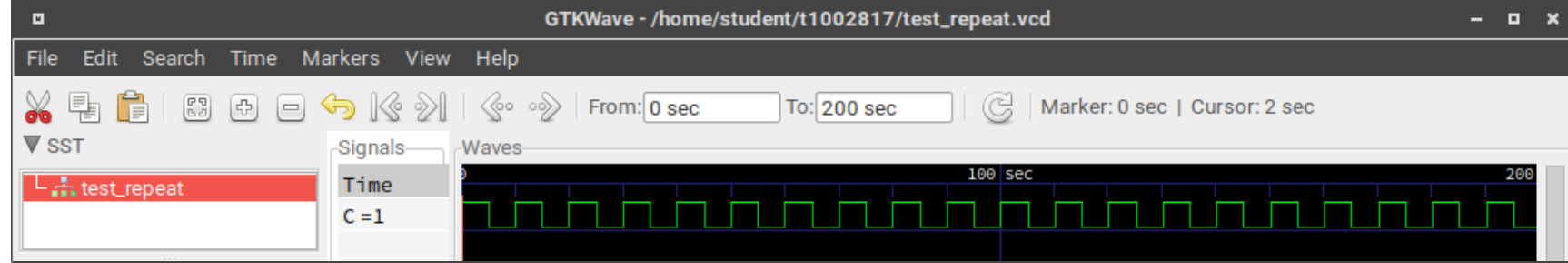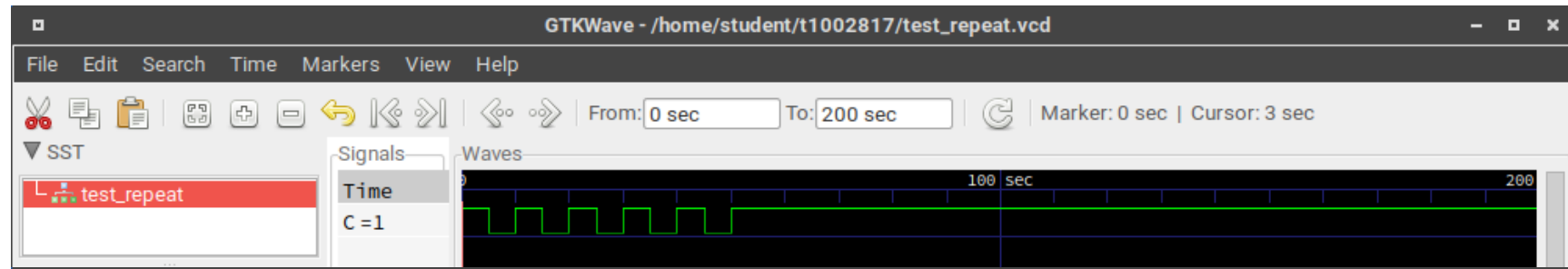
```
initial begin
  forever begin
    repeat (10)
      #5 C = ~C;
    #50;
  end
end
```



Последовательные операторы: циклы forever и repeat (2)

```
initial begin
  forever begin
    repeat (10)
      #5 C = ~C;
    #50;
  end
end
```

 
```
initial begin
  forever begin
    #50;
    repeat (10)
      #5 EC = ~EC;
    end
  end
end
```




Последовательные операторы: цикл for

```
output reg [3:0] Q;  
...  
always @(posedge C) begin  
    Q[3] <= Q[2];  
    Q[2] <= Q[1];  
    Q[1] <= Q[0];  
    Q[0] <= D;  
end
```
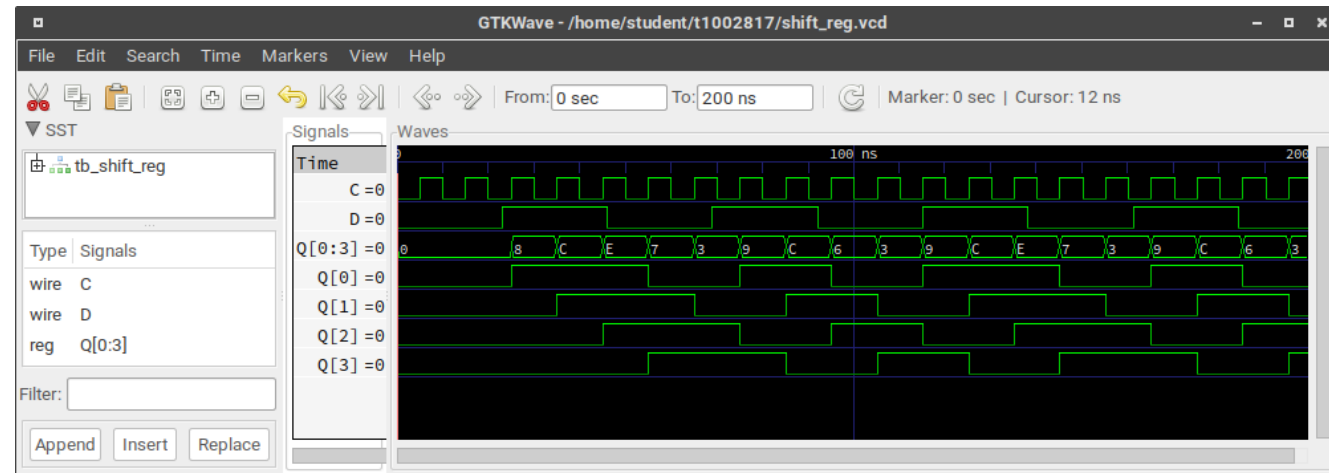
```
integer i;  
always @(posedge C) begin  
  
    for(i = 3; i > 0; i = i - 1)  
        Q[i] <= Q[i - 1];  
  
    Q[0] <= D;  
  
end
```



 Параллельные операторы: позиционное и ассоциативное назначение портов



```
module device(x1, x2, y);  
  input  x1, x2;  
  output y;
```

```
  wire s1, s2;
```

```
  inv  i1(x2, s1);  
  and2 a1(x1, s1, s2);  
  inv  i2(s2, y);
```




```
  inv  i1(.x(x2), .y(s1));  
  and2 a1(.x1(x1), .x2(s1), .y(s2));  
  inv  i2(.x(s2), .y(y));
```

```
  and2 a1(.x2(s1), .y(s2), .x1(x1));
```

```
endmodule
```

 Параллельные операторы: инстанцирование модулей (1)



```
module device(x1, x2, y);  
  input  x1, x2;  
  output y;
```

```
  wire s1, s2;
```

```
  inv  i1(x2, s1);  
  inv  i2(s2, y);  
  and2 a1(x1, s1, s2);
```




```
  inv  i1(x2, s1),  
      i2(s2, y);  
  and2 a1(x1, s1, s2);
```

```
endmodule
```

Параллельные операторы: инстанцирование модулей (2)

```
module tb_device;  
  reg x1, x2;  
  wire y;
```

```
device i1(.x1(x1), .x2(x2), .y(y));
```




```
device i1(.*);
```

```
always #5 x1 = ~x1;  
always #10 x2 = ~x2;
```

```
initial begin  
  $dumpfile("device.vcd");  
  $dumpvars(1, tb_device);  
  x1 = 0;  
  x2 = 0;  
  #100  
  $finish;  
end
```

```
endmodule
```

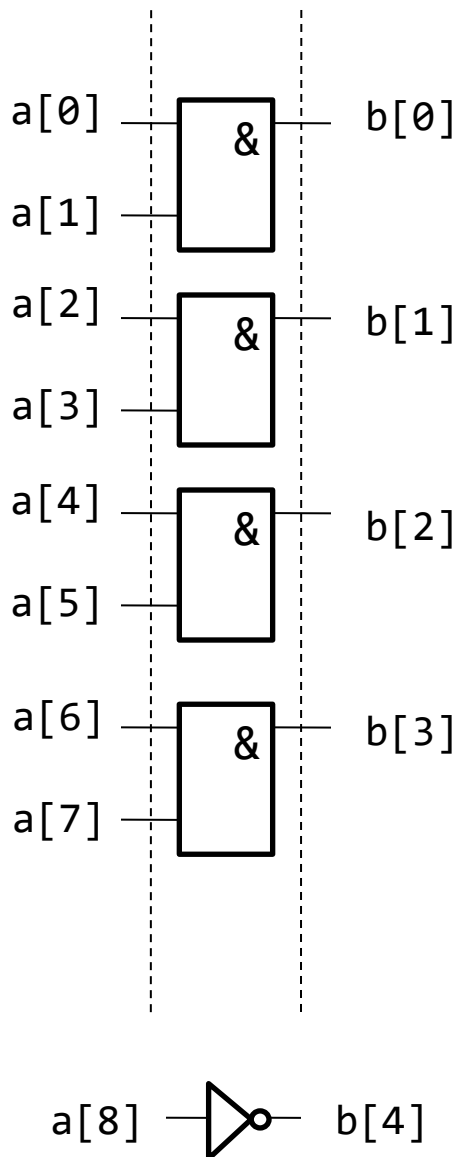Параллельные операторы: оператор generate (1)



Структурное описание:

```
input  [8:0] a;  
wire   [4:0] b;
```

```
genvar g;
```


```
generate
```

```
  for (g = 0; g < 4; g = g + 1)  
    and2 i(a[g*2], a[g*2 + 1], b[g]);
```

```
endgenerate
```

```
inv i1(a[8], b[4]);
```

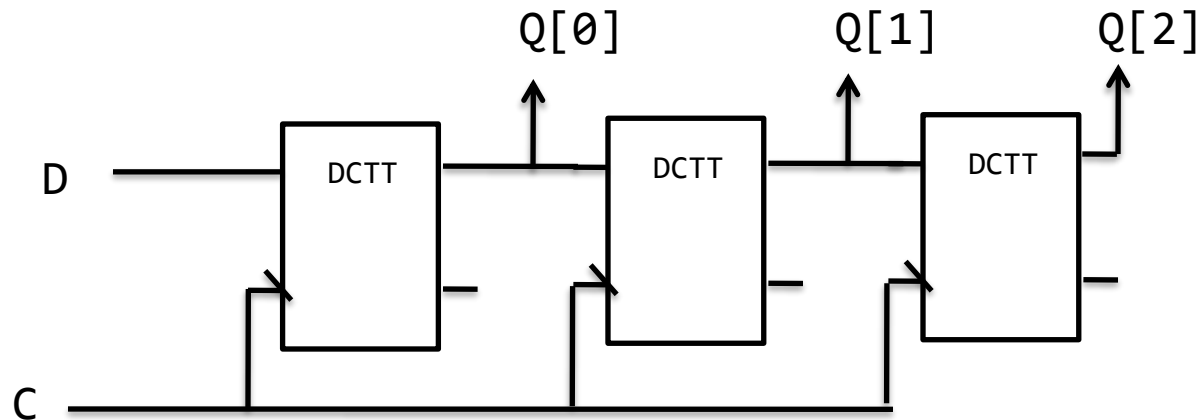Параллельные операторы: оператор generate (2)



```
genvar g;
```

```
dctt i1(.d(D), .c(C), .q(Q[0]), .nq());
```


```
generate
```

```
for (g = 1; g < 3; g = g + 1)
```

```
    dctt i(.d(Q[g - 1]), .c(C), .q(Q[g]), .nq());
```

```
endgenerate
```

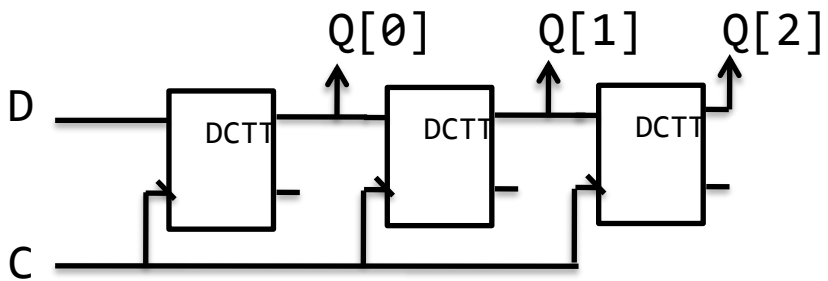Параллельные операторы: оператор generate (3)



```
genvar g;
```

```
generate
```

```
for (g = 0; g < 3; g = g + 1)
```

```
  if (g == 0)
```

```
    dctt i1(.d(D), .c(C), .q(Q[g]), .nq());
```

```
  else
```

```
    dctt i(.d(Q[g - 1]), .c(C), .q(Q[g]), .nq());
```

```
endgenerate
```

Автоматизация запуска: скрипты bash

```
#!/usr/bin/bash
```

```
if [ -f ./a.out ]; then  
    rm ./a.out  
fi
```

```
iverilog -c ./config.cmd  
if [ -f ./a.out ]; then  
    ./vvp a.out  
    gtkwave ./inv.vcd  
else  
    echo -e "\e[31m Verilog code compilation error!\e[0m"  
fi
```

```
● student@localhost:~/t1002817> ./run.sh  
tb_inv.v:5: error: Unknown module type: in  
2 error(s) during elaboration.  
*** These modules were missing:  
        in referenced 1 times.  
***  
Verilog code compilation error!  
○ student@localhost:~/t1002817> █
```


Автоматизация запуска: синтаксис Makefile

all: analyze run view

```
analyze: ./shift_reg.v ./tb_shift_reg.v
    @echo "Erasing simulation results"
    rm -f ./shift_reg.out
    rm -f ./shift_reg.vcd
    @echo "Analyzing design..."
    iverilog -o ./shift_reg.out \
        ./shift_reg.v \
        ./tb_shift_reg.v
```

```
run: ./shift_reg.out
    vvp ./shift_reg.out
```
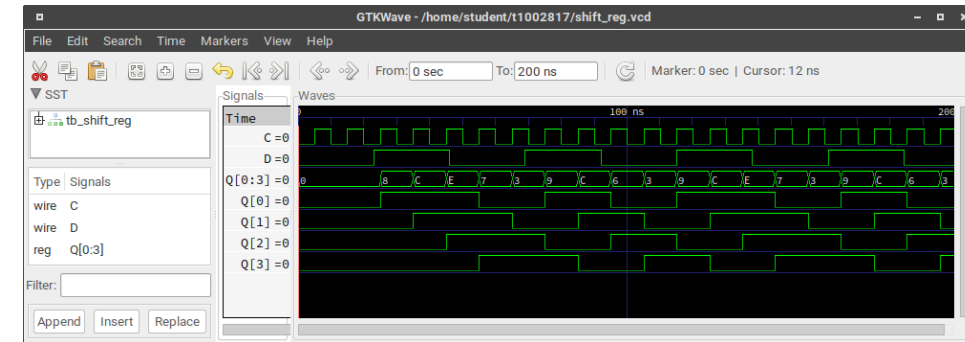
```
view: ./shift_reg.vcd
    gtkwave ./shift_reg.vcd
```



```
student@localhost:~/t1002817> make
Erasing simulation results
rm -f ./shift_reg.out
rm -f ./shift_reg.vcd
Analyzing design...
iverilog -o ./shift_reg.out ./shift_reg.v ./tb_shift_reg.v
./tb_shift_reg.v:7: error: Unknown module type: shft_reg
2 error(s) during elaboration.
*** These modules were missing:
    shft_reg referenced 1 times.
***
make: *** [Makefile:8: analyze] Error 2
student@localhost:~/t1002817> █

student@localhost:~/t1002817> make
Erasing simulation results
rm -f ./shift_reg.out
rm -f ./shift_reg.vcd
Analyzing design...
iverilog -o ./shift_reg.out ./shift_reg.v ./tb_shift_reg.v
vvp ./shift_reg.out
VCD info: dumpfile shift_reg.vcd opened for output.
gtkwave ./shift_reg.vcd
```

GTKWave Analyzer v3.3.104 (w)1999-2020 BSI

```
[0] start time.
[200] end time.
```